

FIG. 1. SCHEMATIC DIAGRAM of the RF wattmeter. Parts with the same function in both sides of the circuit ( $C_1$  and  $C_2$ , etc.) should be matched in actual value, as described in the text. This circuit was used in W8DLD's SSB-600 linear amplifier described in the March-April, 1961 issue.

## TABLE I — PARTS LIST

- $C_1, C_2$ ....1.0-3.5 mmf ceramic trimmers (Centralab 820-D, or equivalent).  
 $C_3, C_4$ ....200-mmF 600-volt miniature disc ceramic.  
 $C_5, C_6$ ....01-mfd. 600-volt disc ceramic.  
 $D_1, D_2$ ....general purpose diodes (1N34A, 1N48, etc.).  
 $J_1, J_2, J_3, J_4$ ....midget phono jacks.  
 $J_5, J_6$ ....chassis type coaxial cable jack (SO-239).  
 $L_1$ ....No. 10 or 12 bare copper wire, 3 inches long, covered with  $\frac{3}{8}$ -inch O.D. copper tubing  $1\frac{1}{2}$  inches long.  
 $L_2$ ....Approximately 48 turns of No. 22 enameled wire on toroid form; see footnote (3).  
 $L_3$ ....35 turns, No. 22 enameled wire over  $L_1$ ; see text for details.  
 $M_1$ ....0 — 150-microampere DC meter; or, see TABLE II for other meter ranges (G. E. DW-91,  $2\frac{1}{2}$  inches; DO-91,  $3\frac{1}{2}$  inches, or equivalent).  
 $R_1, R_2$ ....20 ohms, 1 watt composition.  
 $R_3$ ....linear taper potentiometer; see TABLE II for value.  
 $R_4$ ....1-watt composition resistor; see TABLE II for value.  
 $RFC_1, RFC_2$ ....1 mh single pi-wound RF choke (Miller No. 72F103AP, or equivalent).  
 $S_1$ ....single pole, double throw slide switch (H. H. Smith No. 516, or equivalent).

### MECHANICAL PARTS NEEDED:

- Box, wattmeter — Bud Minibox No. CU-2101A.  
Box, meter — Bud sloping meter case No. CMA-2065 or CMA-2066.  
Dial plate for  $R_3$  — 0-10 markings, 300 degrees, Mallory No. 380.  
8-connection terminal strip — Cinch-Jones No. 56A.

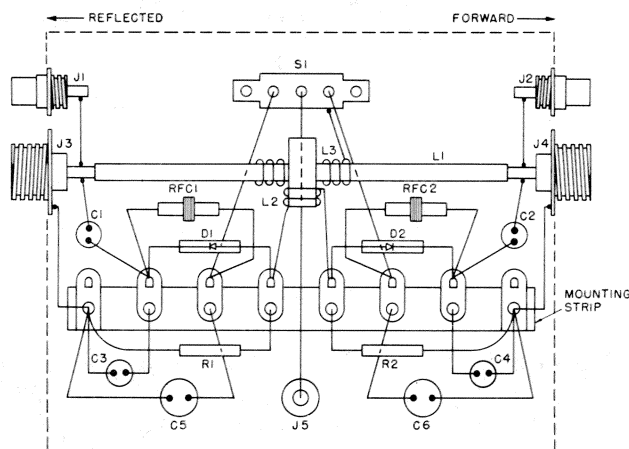


FIG. 2. PARTS LAYOUT for the RF wattmeter. This layout should be followed closely to achieve accurate reflected power readings. NOTE: Either end of the pickup unit may be connected to the transmitter or load, since the circuit is bilateral. The ends have been labelled here for discussion purposes.

## LOW-COST RF WATTMETER (continued from page 1)

able. This makes possible physically small fixed larger capacitances for  $C_3$  and  $C_4$  to overcome the problem of stray RF voltage pickup by these capacitors.

It was previously mentioned that this device is really two wattmeters in one case. Obviously this suggests that any time two components with the same value are specified in TABLE I — PARTS LIST they should match each other closely in value. For example, the 20-ohm, 1-watt diode load resistors ( $R_1$  and  $R_2$ ) may measure from 15 to 30 ohms, but they must both read the same resistance. This also applies to the 200-mmF ceramic capacitors. From 150 to 250 mmf will work fine if the capacitances are matched. Although 1N34A diodes are specified, more important than the type of diode, they should match each other in forward and reverse characteristics. This will enable the RF wattmeter to read the same regardless of which direction it is connected in the coaxial line.

The toroid wound current transformer is a problem to shield by an ordinary method, so why not shield the primary of the transformer from its secondary? This is almost quicker done than said! Slip a piece of tubing or put some tape on the center conductor. Wind a tight winding of

<sup>1</sup>"The Monimatch," by L. G. McCoy, W1ICP, QST, October, 1956, page 11. Also, "The Monimatch — Mark II," L. G. McCoy, QST, February, 1957, page 38.

<sup>2</sup>"An Inside Picture of Directional Wattmeters," by W. B. Bruene, W0TKK, QST, April, 1959, page 24.

<sup>3</sup>Part No. 57-1541, Radio Cores, Inc., 9540 South Tully, Oak Lawn, Ill.

<sup>4</sup>"Not Just a Novelty," — by Davis A. Helton, W0PME, QST, January, 1961, pages 21 to 25.

## presents HOW-TO-DO-IT IDEAS from the 999 radio amateurs at GENERAL ELECTRIC

A bi-monthly publication of the RECEIVING TUBE DEPARTMENT  
Owensboro, Kentucky, U. S. A. • Editor — E. A. Neal, W4ITC

G-E HAM NEWS is available free from authorized G-E Tube distributors. Some distributors mail copies locally to their customers.

A low-cost direct-mail subscription plan is available to persons residing in the United States and its possessions (including APO and FPO numbers). Subscription rates are:

One Year (6 issues).....	\$1.00
Two Years (12 issues).....	\$2.00
Three Years (18 issues).....	\$3.00
Five Years (30 issues).....	\$4.00

Enclose check or money order for U. S. currency for the proper amount above made payable to "General Electric Company."

Residents of Canada may subscribe to G-E HAM NEWS for \$1.00 per year from the Canadian General Electric Company, Ltd., Electronic Tube Market-

ing Section, 189 Dufferin Street, Toronto 3, Ontario, Canada. Enclose check or money order made payable to: "Canadian General Electric Company, Ltd."

Distribution of G-E HAM NEWS in more than 40 foreign countries is handled through the International General Electric Company. A listing of outlets is available from the G-E HAM NEWS office. Or, write to: Customer Inquiry Section, International General Electric Company, 150 East 42nd Street, 7th Floor, New York 17, New York, U. S. A.

NOTE: The disclosure of any information or arrangements herein conveys no license under any patents of General Electric Company or others. In the absence of an express written agreement to the contrary, the General Electric Company assumes no liability for patent infringement (or any other liability) arising from the use of such information by others.